

Total No. of Printed Pages:2

**SUBJECT CODE NO:- H-433**  
**FACULTY OF SCIENCE AND TECHNOLOGY**  
**S.E. (CSE/IT)**  
**Digital Electronics**  
**(REVISED)**

[Time: Three Hours]

[Max.Marks: 80]

Please check whether you have got the right question paper.

- N.B
1. Q.1 and Q.6 are compulsory.
  2. Solve any two questions from Q.2 to Q.5 and any two questions from Q.7 to Q.10.

**Section A**

- Q.1 Solve any five questions: 10
- a) State and prove De-Morgan's theorem.
  - b) Represent  $(-33)_{10}$  in
    - i) Sign Magnitude
    - ii) One's complement
  - c) Convert following-
    - i)  $(9AC.FA)_{16} = (?)_8$
    - ii)  $(19.625)_{10} = (?)_2$
  - d) Design a 4 i/p NAND gate by using 2 i/p NAND gates only.
  - e) What is mean by self-complementing codes?
  - f) Reduce following using k map.  
 $F(A,B,C) = \sum m(1,2,3,7)$
  - g) Perform following binary arithmetic operations
    - i)  $(111\ 0101) / (1001)$
    - ii)  $(1001) * (1101)$
  - h) Realize the following expression using logic gates  
 $Y = (\bar{A} \cdot \bar{B} \cdot \bar{C}) + (A \oplus B) + (A \cdot C)$
- Q.2
- a) Implement 3 input NAND gate using TTL logic. 07
  - b) Differentiate between analog signal and digital signal. 08
- Q.3
- a) Define weighted codes, excess-3 code, BCD and define gray code. Explain with example. 07
  - b) Use NOR gate to produce AND, OR, NOT, NAND, X-OR and X-NOR gates. 08

- Q.4 a) Design binary to gray code converter. 07  
 b) What is digital signal? Explain its different characteristics. 08
- Q.5 a) Design a BCD to 7 segment decoder. 07  
 b) Design a 4 bit adder with look ahead carry. 08

**Section B**

- Q.6 Solve any five questions: 10  
 a) What is Demultiplexer? Explain with any one example.  
 b) Explain Decimal to BCD Encoder.  
 c) What is PROM?  
 d) What is the logic symbol and truth table of T F/F?  
 e) Compare combinational and sequential circuits.  
 f) Draw logic diagram for 4 bit PIPO shift reg.  
 g) Draw 3 bit asynchronous counter.  
 h) Write excitation table of SR F/F.
- Q.7 a) Design and implement circuit for 2 bit comparator using 4 line to 16 line decoder and multi input OR gates. 08  
 b) Draw and explain NAND implementation of 1 bit memory cell. 07
- Q.8 a) Design 16:1 multiplexer using two 8:1 multiplexer and logic gates. Explain working. 08  
 b) Draw logic diagram of 4 bit SISO right shift register. Explain it. 07
- Q.9 a) Convert 08  
 i) SR F/F to JK F/F.  
 ii) D type F/F to JK F/F  
 b) Design and explain MOD-10 ripple counter. 07
- Q.10 a) Explain designing of n bit comparator using IC. 08  
 b) Explain working of 4 bit universal shift register. 07