

**CODE NO:- K-8014**  
**FACULTY OF ENGINEERING AND TECHNOLOGY**  
**M.E.(Electrical Power Systems) Examination Nov/Dec 2015**  
**Advanced Power Electronics**  
**(Revised)**

[Time: Three Hours]

[Max. Marks: 80]

“Please check whether you have got the right question paper.”

- N.B
- i) Solve any two questions from each section
  - ii) Use suitable data if required.

## SECTION-A

- Q.1
- a) State the various types of turn on methods of SCR .which is the universal method & why? 10
  - b) Discuss the switching characteristics of IGBT with the help of neat circuit diagrams & waveforms. 10
- Q.2
- a) Show that the performance of a three phase full converter as influenced by source inductance is given by the relation:  $\cos(\alpha + \mu) = \cos\alpha - \frac{\omega L_s I_d}{E_m}$  10  
 Were  
 $\alpha$  is the firing angle       $\mu$  – overlap angle  
 $L_s$ - source inductance     $I_d$  – load current  
 $E_m$  – peak value of source voltage  
 $\omega$ –angular freq. (rad/sec)
  - b) A angle phase full converter supplies an inductive load. Supply voltage is 230v, 50Hz & the firing angle is  $50^\circ$ . Assuming that the output current is continuous & ripple free & equal to 15amp. Determine 10
    - i) Average output volt
    - ii) Input power factor
- Q.3 Write short notes (any two) 20
- i) Principle of operation CUK converter
  - ii) Dual converter
  - iii) Operating principle of GTO.

## SECTION-B

- Q.4 With the help of neat circuit diagram & waveform explain the operation of transistorized three phase bridge inverter with resistance load in  $180^\circ$  conduction mode. 20
- Q.5
- a) What is pulse width modulation? List the various pwm techniques. Explain any one of them. 10
  - b) Draw & explain the various types of zero current switch topology. 10
- Q.6
- a) Explain with neat circuit diagram & waveform the operation of full bridge zvs pwm converter 10
  - b) Write a short note on parallel resonant converter source 10