

Total No. of Printed Pages:2

**SUBJECT CODE NO: H-1613**  
**FACULTY OF ENGINEERING AND TECHNOLOGY**  
**ME (Electrical Power Electronics)**  
**Advanced Power Electronics**  
**(REVISED)**

[Time: Three Hours]

[Max.Marks:80]

Please check whether you have got the right question paper.

- N.B
- i. Solve any two questions from each section.
  - ii. Use suitable data if required.

**Section A**

- Q.1
- a) State the various types of turn – on methods of SCR. Which is the universal method? Why? 10
  - b) What are the peripheral effects of power electronics system? Suggest methods to mitigate the same. 05
  - c) With neat diagram and waveforms, explain the control characteristics of IGBT. 05
- Q.2
- a) Explain the principle of ON – OFF and phase control of Ac voltage regulators. 10
  - b) Show that the performance of three phase full converter as influenced by source inductance is given by the relation:  $\cos(\alpha + \mu) = \cos\alpha - \frac{W L_s I_d}{E_m}$  10
- Where:  
 $\alpha$  is the ring angle  
 $\mu$  is the overlap angle  
 $L_s$  - source Inductance  
 $I_d$  - load current  
 $E_m$  - peak value of source voltage  
 $W$  - angular frequency (rad / Sec)
- Q.3 Write short Notes on any two:- 20
- i) Principle of operation of Buck converter.
  - ii) Six pulse circulating current conducting Dual converter
  - iii) Methods of power factor improvement in controlled rectifiers

**Section B**

- Q.4
- a) Describe in detail the techniques for optimizing the base drive of a BJT. 10
  - b) Explain the operation of six – step inverter and obtain the expression for output voltage in terms of d.c. supply voltage  $V_d$ , with the help of neat diagram. 10

- Q.5 a) Draw and explain the various types of zero current switch topology. 10
- b) What is resonant converter? Explain the operation of parallel resonant converter. 10
- Q.6 a) Explain with neat circuit diagram and waveform the operation of full bridge ZVS PWM converter. 10
- b) Explain the circuit operation and equivalent circuits of series resonant inverter. 10