

Total No. of Printed Pages:2

**SUBJECT CODE NO: H-1613**  
**FACULTY OF SCIENCE AND TECHNOLOGY**  
**M.E. (Electrical Power Electronics)**  
**Advanced Power Electronics**  
**(REVISED)**

[Time: Three Hours]

[Max.Marks:80]

Please check whether you have got the right question paper.

- N.B
- i. Solve any two questions from each section.
  - ii. Use suitable data if required.

**Section A**

- Q.1
- a) With neat diagram and waveforms, explain the control characteristics of GTO. 05
  - b) Discuss the switching characteristics of IGBT with the help of neat circuit diagrams & waveforms. 10
  - c) Explain the switching characteristics of MOSFET. Draw its transient model. 05
- Q.2
- a) Show that the performance of a three phase full converter as influenced by source inductance is given by the relation:  $\cos(\alpha + \mu) = \cos\alpha - \frac{W L_s I_d}{E_m}$  10  
 Where:  
 $\alpha$  = ring angle  
 $\mu$  = overlap angle  
 $L_s$  = source Impedance  
 $I_d$  = load current  
 $E_m$  = peak value of source voltage  
 $W$  = angular frequency (rad / Sec)
  - b) What is the principle of phase control? Also derive the performance parameters of a single phase full wave a.c. controller with RL load. 10
- Q.3 Write short Notes on any two:- 20
- i) Dual converter
  - ii) Effect of source and load inductances on voltage – controllers
  - iii) Principle of operation of Boost converter

**Section B**

- Q.4 With the help of neat circuit diagram and waveform, explain the operation of transistorized three phase Bridge inverter with resistance load in **180°** conduction mode. 20
- Q.5
- a) Write the drawback of SPWM. Also describe and suggest other techniques offering improved performance with waveforms. 10
  - b) Explain the operation of ZVS: resonant converter 10

- Q.6 Write short notes on any two:
- i) Operation of resonant DC link inverter.
  - ii) Load commutated inverters
  - iii) Working principle of single phase CSI.