

“Please check whether you have got the right question paper.”

- i) Q. No.1 and Q.No.6 are compulsory.
- ii) Attempt from each section any two questions from remaining questions.
- iii) Assume suitable data wherever necessary.
- iv) Figures to the right indicate full marks

**SECTION-A**

- Q.1 Solve Any five 10
- a) Draw the output characteristics of CB mode and label all variables.
  - b) List advantages and disadvantages of FET over bi-polar Transistor.
  - c) Draw the symbol of PNP and NPN Transistor and label.
  - d) List applications of comparator.
  - e) What is multivibrator?
  - f) Define voltage regulation?
  - g) What is zero-crossing detector?
  - h) Draw the circuit diagram of integrator.
- Q.2 a) With the neat diagram explain the working of two-stage Rc-coupled amplifier . 08  
 b) Compare CB,CC and CE configuration of BJT amplifier. 07
- Q.3 a) Draw the block diagram of operational amplifier and explain it in details . 08  
 b) Draw and Explain with suitable circuit diagram and wave forms the schmitt-trigger using op-amp. 07
- Q.4 a) Explain pin-diagram of IC555 with neat sketch. 07  
 b) What is peak detector ? Explain with circuit diagram and output wave forms . 08
- Q.5 Write short note on (any three) 15
- a) Instrumentation Amplifier
  - b) Active filter
  - c) V to I convertor
  - d) Class –A Amplifier .

**SECTION-B**

- Q.6 Solve any five 10
- a) What are logic gates ?
  - b) Convert 0.640625 decimal number in its octal equivalent.
  - c) Realize using logic gates given Boolean function  $.y=ABC+B\bar{C}D + \bar{A}BC$
  - d) Construct the K-map for the following truth table
- | Input |   | o/p |
|-------|---|-----|
| 0     | 0 | 0   |
| 0     | 1 | 0   |
| 1     | 0 | 0   |
| 1     | 1 | 1   |
- e) Define up-down counter.
  - f) Give the truth table and graphic symbol of D-flipflop
  - g) Define MUX and Draw the symbol for 2:1 MUX.
  - h) Define static and dynamic RAM.

- Q.7 a) Use K-map to minimize the following sop expression.  $ABCD + ABC\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + A\bar{B}CD + \bar{A}\bar{B}C\bar{D} + ABC\bar{D} + A\bar{B}C\bar{D}$ . 08
- b) Explain the operation of J-K Flip, Flop with logic diagram and truth table . 07
- Q.8 a) Represent decimal no. 8620 in 08
- i) BCDcode
  - ii) Excess-3code
  - iii) Hexedecimal
  - iv) Octal no
- b) Design 4-bit up-down Counter. 07
- Q.9 a) With the help of neat sketch explain 8:1 multiplexer with truth table. 08
- b) Explain the operation of PROMS and EPROMS. 07
- Q.10 Write short note on (Any three) 15
- a) Shift Registers
  - b) Demorgon's theory
  - c) Gray code
  - d) Twisted ring counter.