

SUBJECT CODE NO:- P-247
FACULTY OF ENGINEERING AND TECHNOLOGY
S.E. (EEP/EE/EEE) Examination May/June 2017
Network Analysis
(Revised)

[Time: Three Hours]

[Max.Marks:80]

Please check whether you have got the right question paper.

- N.B
- i) Use suitable data if required.
 - ii) Q.No.1 from section A and Q.No.6 from section B are compulsory.
 - iii) Solve any two questions from the remaining questions in each section A and B.

Section A

- Q.1 Solve any five (2x5) 10
- i. Define convolution integral.
 - ii. State the Thevenin theorem.
 - iii. Define linear and nonlinear network.
 - iv. Give principle of duality
 - v. What are magnetically coupled circuits.
 - vi. State compensation theorem.
 - vii. What is significance of critical conditions
 - viii. Define and give characteristics of unit step function
- Q.2 A Write short note on duality and dual network 05
- B Compute the voltage v for the coupled circuit in fig.1 05

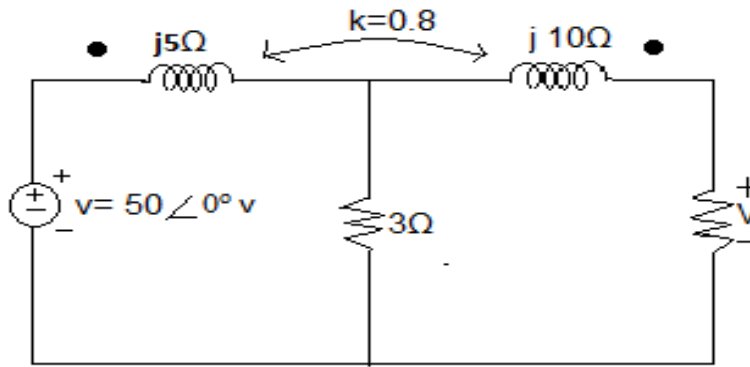


Fig 1

- C Replace the network at terminals A-B with Thevenin equivalent circuit. 05

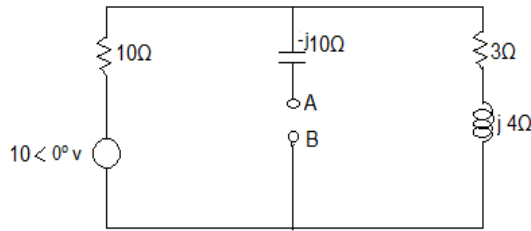


Fig 2

- Q.3 A Find how many seconds after $t=0$ has the current $i(t)$ become one half of its initial value in the given circuit in fig 3 05

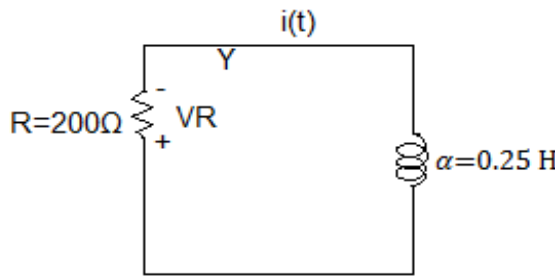


Fig 3

- B The switch is closed $t=0$ find value of $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$ at $t=0^+$. Assume initial current of inductor to be zero. 05


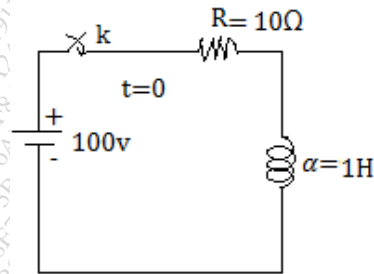


Fig 4

- C Find out the Laplace transform of $f(t) = e^{-at}$ for $t \geq 0$. 05

Q.4 A Find the Laplace transform of the waveform shown in fig.5

05

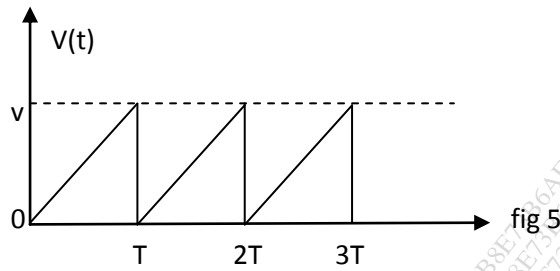

B Find inverse Laplace transform of given F(s)

05

$$F(s) = \frac{s+2}{s(s+3)(s+4)}$$

C Obtain the inverse Laplace transform of given F(s)

05

$$F(s) = \frac{s-2}{s(s+1)^3}$$

Q.5 A Write the advantages of s domain network.

05

B Derive the transform impedance and of induction and capacitor.

05

C Find the dimming point impedance of the given one port network shown in fig 6.

05

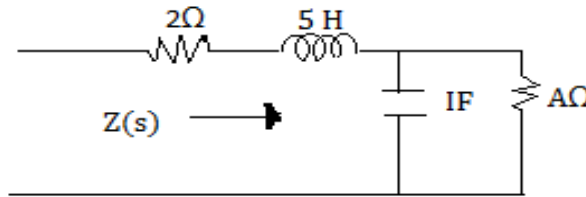


Fig 6

Section B

Q.6 Solve any five

10

- i. Define pole and zero of a network function.
- ii. Write the Y parameter of two port network.
- iii. Define RMS value of an alternating quantity.
- iv. List the network function of two port n/w
- v. Test whether the following represent driving point immittances $\frac{S^2+3S+2}{S^2+6S+9}$.
- vi. What is complex frequency?
- vii. What is Fourier series? What are the applications of Fourier transform.
- viii. What is physical significance of reactive power?

Q.7 A If $I(s) = \frac{3s(s+2)}{(s+1)(s+4)}$ plot poles and zeros in s plane and obtain time domain response i(t)

05

B Plot the poles and zeros of the network function $F(s) = \frac{s(s+1)}{(s+3)(s^2+4s+5)}$

05

C Derive the inter conversion to connect h parameter into z parameters.

05

2017

Q.8 A Find h parameters for the network

05

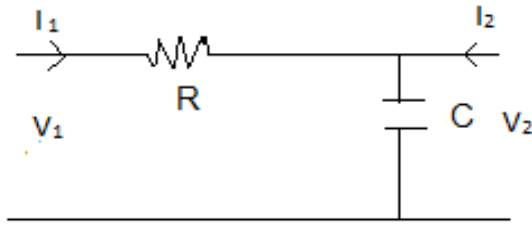


Fig 7

B State the limitations on pole and zero location in transfer function of two port network.


05

C What is the power transfer optimization what are the problems in optimizing power transfer

05

Q.9 A Find the Fourier coefficients of waveform f (t).

05

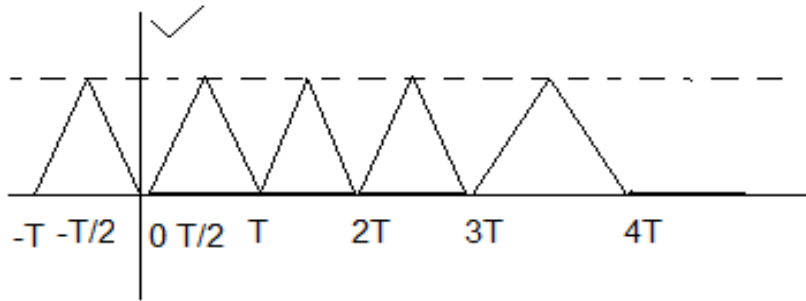

B Write short note on insertion loss


05

C Explain in detail average power and complex power.

05

Q.10A Find the network functions $\frac{V_2}{I_1}$ for the network fig. 9


05

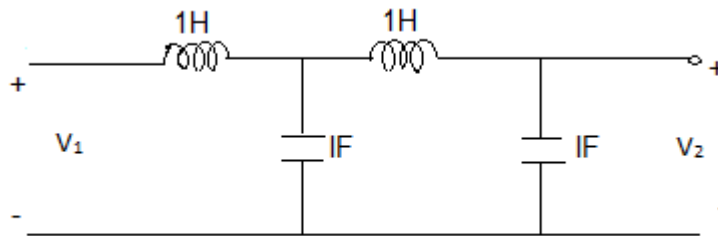

B For the following network show.

05
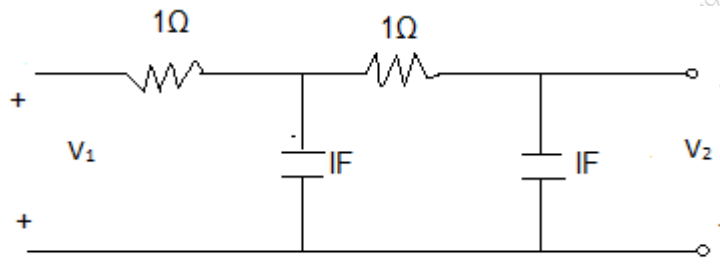
$$\frac{v_2}{v_1} = \frac{1}{s^2 + 3s + 1}$$



C Write short note on half wave symmetry.