

SUBJECT CODE NO:- P-390
FACULTY OF ENGINEERING AND TECHNOLOGY
S.E. (EEP/EE/EEE) Examination MAY/JUNE-2016
Network Analysis
(Revised)

[Time: Three Hours]

[Max Marks:80]

“Please check whether you have got the right question paper.”

N.B


- i) Q.No.1 from section A and Q.No.6 from section B are compulsory.
- ii) Attempt **any two** questions from the remaining questions in each section.
- iii) Assume suitable data, if necessary.

Section A

Q.1 Solve **any five**

10

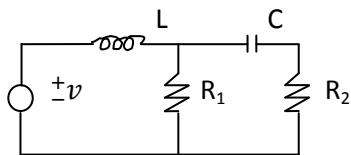- a) Enlist the applications of Laplace transform
- b) Draw the dual of the network



- c) Find the Laplace of following function t^2
- d) Define and give characteristics of unit ramp function
- e) State the superposition theorem
- f) Define convolution integral
- g) Write the feature of Laplace transform
- h) What is super node

Q.2 a) State and prove the Mailman theorem

05

- b) Obtain the Thevenin equivalent circuit across a-b of the circuit in fig. 1

05

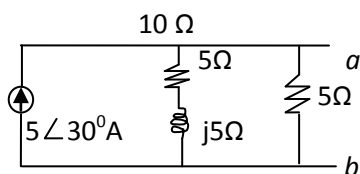


fig.1

- c) Find the current through capacitor using superposition in fig. 2

05

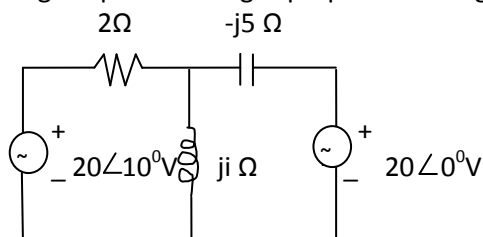


Fig. 2

Q.3 a) Find i_1 and i_2 from the circuit in fig 3

05

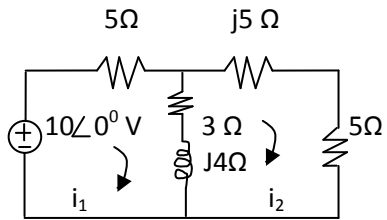


Fig. 3

b) In the network of fig. 4 find the impedance as seen from A & C if $Z_L = 10 - j10\Omega$

05

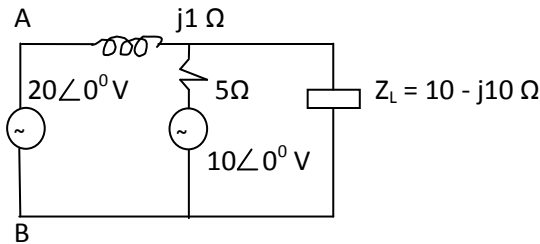


Fig. 4

c) State and explain reciprocity theorem

05

Q.4 a) Find the Laplace transform of the function in fig. 5

05

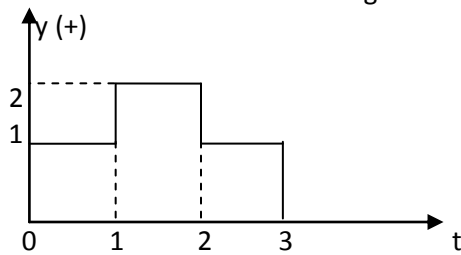


Fig. 5

b) Find the inverse Laplace transform of the following functions

05


$$\frac{S^2/S + 3}{(S + 1)(S + 4)^2}$$

c) A series RLL circuit with $R = 5\Omega$, $\alpha = 0.1\text{H}$ and $C = 500\text{uf}$ has a constant voltage $V = 10\text{V}$ applied $t = 0$ find resulting current

05

Q.5 a) Find the Laplace Transform of non-periodic function in fig. 6

05

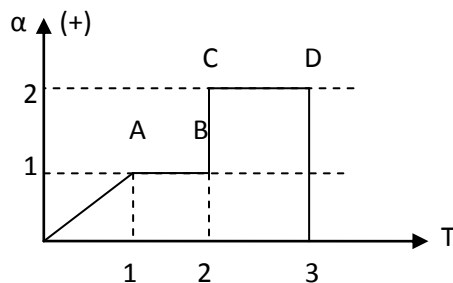

b) Explain the concept of source transformation in the analysis of the electrical networks

05

c) Explain with neat circuit diagram dot convention

05

Section B


Q.6 Solve **any five**

10

- a) What is a two port network
- b) Write the z parameters for two port network
- c) What is the physical significance of reactive power
- d) Write Y parameter in terms of Z parameters
- e) What is Fourier series? What are the applications of Fourier transform
- f) Define RMS value of an alternating quantity
- g) Define stability of a active network
- h) Draw the T-network and Ladder n/w

Q.7 a) Find the driving point impedance and its poles and zeros in fig. 7

05

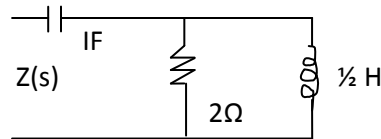


- b) State all the instruction on pole zero location for transfer function
- c) Derive the inter conversion to convert h parameters into y parameters

05

05

Q.8 a) Find ABCD parameters for the circuit in fig 8.

05

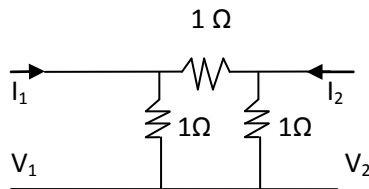

b) A typical two port network is characterized the following eq.

05

$$2V_1 + 4 I_2 = I_1$$

$$V_2 + 6 V_1 = 8 I_2$$

Find the values of y_{11} and z_{21}


c) For the given network function draw pole zero plot and obtain time response $i(+)$

05

$$I(s) = \frac{2s}{(s + 1)(s + 2)}$$

Q.9 a) Obtain the Fourier series of the waveform in fig. 9

05

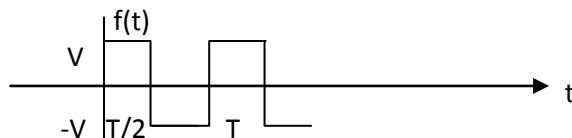

- b) Write short note on stability of active networks
- c) What are the problems in optimizing power transfer

05

05

Q.10a) Explain in brief concept of even and odd functions

05

b) For the network show that $\frac{v_2}{v_1} = \frac{2s}{7s^2+7s+5}$

05

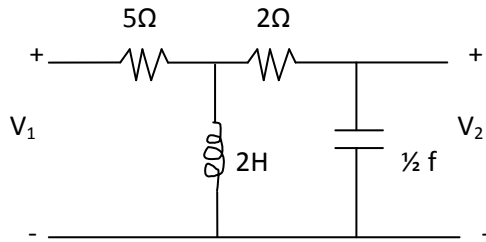


Fig. 10

c) Find network function $\frac{V_2}{V_1}$ for the network in fig. 11

05

