

SUBJECT CODE NO:- P-298
FACULTY OF ENGINEERING AND TECHNOLOGY
T.E.(EEP/EE/EEE) Examination MAY/JUNE-2016
Power Electronics
(Revised)

[Time: Three Hours]

[Max Marks:80]

“Please check whether you have got the right question paper.”

- N.B
- 1) Q.No.1 & 6 are compulsory.
 - 2) Solve any two questions form remaining from each section.
 - 3) Draw neat waveforms wherever necessary.
 - 4) Assume suitable data if required.

Section A

- Q.1 Solve any five. 10
- a) What are the different methods to turn on the thyristor?
 - b) Define: - i) Latching current & ii) holding current of thyristor.
 - c) What are the differences between MOS FET & IGBT?
 - d) What are the advantages of freewheeling diode in controlled rectifier?
 - e) What are the differences between fully controlled & half controlled rectifiers?
 - f) State the performance parameters of controlled rectifier.
 - g) What do you mean by dc chopper?
 - h) What are the advantages of dc chopper over controlled rectifiers?
- Q.2 07
- a) Explain with neat circuit the triggering requirements of IGBT.
 - b) Explain the most sensitive operating modes of TRIAC. 08
- Q.3 08
- a) State the controlled rectifier's classification on the basic of quadrant of operation. Explain with neat circuit & waveform the inversion operation of 1- ϕ fully controlled bridge rectifier.
 - b) Single phase full converter delivers a constant load current I_o . Express its source current in Fourier series 07 and derive the expressions for following performance parameters.
- 1) Displacement factors.
 - 2) Power factor.
 - 3) Active & reactive power inputs.
- Q.4 08
- a) Explain principle of operation of time ratio control & current limit control strategies for chopper circuit.
 - b) A step down chopper supplied from dc source of 200V. The load parameter are $R=6\Omega$, $L=10m\ H$ & $E=60V$. 07
The chopper is operating with chopping frequency of 1200Hz & duty cycle of 0.6.
Assuming continuous conduction. Determine.
- i) average load current
 - ii) current ripple
- Q.5 Write short notes. 08
- a) Working of 3-ph fully controlled bridge rectifier. 08
 - b) Dynamic character of SCR. 07

Section B

- Q.6 Solve any five. 10
- a) Why thyristors are not preferred for inverters?
 - b) What are the advantages of PWM control of inverter?
 - c) Draw the circuit diagram of three phases MC Murray bridge inverter.
 - d) What do you mean by switch mode converter?
 - e) What are the four basic types of switching mode regulators?
 - f) What are the performance parameters of a PWM converter?
 - g) What are the effects of chopping frequency on filter sizes?
 - h) A single phase full wave ac voltage controller has a resistive load of $R=10\Omega$ & input voltage is $V_s=100V$, 50Hz. The delay angle of thyristor T_1 & T_2 are $\alpha_1 = \pi/2$ & $\alpha_2 = \pi + \frac{\pi}{2}$ respectively. Determine
 - a) The rms value of output voltage V_o
 - b) Average input current.
- Q.7 10
- a) Explain with neat circuit diagram the 120° mode operation of 3-ph VSI. 10
 - b) State the different voltage control methods used to control the output voltage of inverter. Explain internal gain control method. 05
- Q.8 07
- a) What is PWM? What are its advantages? Explain single pulse width modulation tech. 07
 - b) Explain with neat circuit diagram & waveform the operation of buck-boost converter. 08
- Q.9 10
- a) Prove that the peak to peak ripple current for buck converter is given by 10
$$\Delta I = \frac{V_s k (1 - k)}{f L}$$
 - b) List out the applications of PWM diode converters. 05
- Q.10 Write short notes. 08
- a) Three phase to single phase cycloconverter. 08
 - b) Power conditioners. 07