

[Total No. of Printed Pages:2]

**CODE NO:- Z-306**

**FACULTY OF ENGINEERING**

**T.E (EEP/EE/EEE) - Year Examination June – 2015**

**Power Electronics**

**(Revised)**

[Time: Three Hours]

[Max. Marks: 80]

“Please check whether you have got the right question paper.”

- i) Question No. 1 and Question No. 6 are compulsory.
- ii) Solve any two questions from remaining questions of sections A & B
- iii) Draw neat waveforms
- iv) Figures to the right indicate full marks

SECTION A

- Q.1 Answer any five questions 10
- i) What is power electronics?
  - ii) What is the purpose of  $dv/dt$  &  $di/dt$  ratings?
  - iii) What is the on state condition of thyristor
  - iv) What is the meaning of metal oxide in MOSFET?
  - v) What is the important of buffer layer in IGBT?
  - vi) Give the reason for “GTO is a current controlled minority carrier device”
  - vii) Define ideal switch & practical in case of power electronic devices.
  - viii) Draw the transfer characteristics of MOSFET & IGBT.
- Q.2 a) Draw & explain the switching characteristics of SCR during its turn-on & turn –off process 08  
b) Draw construction features of MOSFET explain its switching characteristics 07
- Q.3 a) How does GTO differ from conventional thyristor? Give the circuit symbol & static V-I characteristics of GTO. Also discuss the turn-off process of GTO 08  
b) In a phase controlled converter has a purely resistive load of R & the delay angle is  $\alpha = \frac{\pi}{2}$ . Determine 07  
a) Rectification efficiency b) form factor c) ripple factor d) TUF (total utilization factor)
- Q.4 a) Discuss how conduction takes place in PMOSFET of n- channel type 08  
b) A 3-phase half-wave controlled converter is fed from 3 phase, 400v 50Hz source & is connected to load taking a constant current of 36A. Thyristors have a constant drop of 1.4v. 07  
a) Calculate average value of load voltage for a firing angle of  $30^\circ$  &  $60^\circ$   
b) Determine average & rms current ratings as well as PIV of thyristors  
c) Find the average power dissipated in each thyristors
- Q.5 a) Explain with neat circuit diagram & waveforms of dual converter 08  
b) In the single phase full converter has a RL load having  $L= 6.5\text{mu}$ .  $R = 0.5\Omega$  &  $E = 10\text{v}$ . the input voltage is  $v_s = 120\text{v}$  at (rms) 60Hz. Determine 07  
a) The load current  $I_{L0}$  at  $wt = \alpha = 60$   
b) The average thyristor current  $I_A$   
c) The rms thyristor current  $I_R$   
d) The rms output current  $I_{rms}$   
e) The average output current  $I_{de}$

## SECTION B

- Q.6 Answer any five questions 10
- i) What is pwm?
  - ii) Define Buck-Boost converter
  - iii) Define voltage source & current source inverter
  - iv) What do you mean by duty cycle & modulation index?
  - v) List out the types of choppers
  - vi) What is the use of freewheeling diode?
  - vii) What is dual converter?
  - viii) List out the different types of converters
- Q.7
- a) State different methods of pulse width modulation technique used in inverter. Explain any one in detail 08
  - b) Explain the control techniques for output voltage of chopper 07
- Q.8
- a) Derive the expression for  $I_o \text{ max}$  &  $I_o \text{ min}$  for class- A chopper. Also derive the expression for per unit ripple factor 08
  - b) The single phase full bridge inverter has the resistive load of  $24 \Omega$  & dc. Input voltage of 48 volts. 07  
Determine
    - a) the rms output voltage at fundamental frequency
    - b) the output power
    - c) the average & peak current of each thyristors
    - d) PIV rating of each thyristor
- Q.9
- a) Explain with neat circuit diagram & waveforms of a step-up & step-down choppers 08
  - b) A step –up chopper has input voltage of 220v & output voltage of 660. If the conducting time of thyristor 07  
chopper is  $100\mu\text{s}$  (microsecond) compute the pulse width of output voltage. In case output voltage pulse width is halved for constant frequency operation, find the average value of new output voltage
- Q.10
- a) What do you mean by cyclo-converter? What are its types? Explain advantages and disadvantages of cyclo 08  
converter state the factors affecting the harmonics in cyclo converter
  - b) Explain four quadrant chopper in detail & modes of quadrant operation 07