

SUBJECT CODE NO:- P-295
FACULTY OF ENGINEERING AND TECHNOLOGY
F. E. (All) (CGPA) Examination May/June 2017
Basic Electronics Engineering
(Revised)

[Time: Two Hours]

[Max.Marks:40]

Please check whether you have got the right question paper.

- N.B
- i) Q.No.1 is compulsory.
 - ii) Attempt any two questions from remaining questions.
 - iii) Assume suitable data if required.
- Q.1 Solve any five 10
- a) Find the color code for the following:-
 - 1) 4.4 k Ω 2) 200 k Ω with $\pm 5\%$ tolerance.
 - b) How depletion layer is formed?
 - c) Draw the symbols for PN Junction diode SCR, TRIC, DZAC.
 - d) What are the different types of capacitors?
 - e) State the need for voltage regulation.
 - f) What is the difference between Zener diode & normal PN junction diode?
 - g) Draw the symbol and truth table for NAND gate and 'AND' gate.
- Q.2 08
- a) What are the different types of MOSFET? Explain any one in detail.
 - b) Explain construction working principles of SCR device. 07
- Q.3 08
- a) Why there is need of filter? Explain any one filter with its input and output wave form.
 - b) Explain any one fixed IC Voltage regulator with its suitable example. 07
- Q.4 08
- a) Describe hexadecimal, octal number system with suitable example.
 - b) Explain AND, OR, and NOT gate with their truth table. 07
- Q.5 Write a short note on following (any three) 15
- a) JFET device
 - b) MOSFET construction
 - c) Regulated DC power supply
 - d) Universal gates
 - e) Applications of rectifiers.