

Time: Two Hours

Maximum Marks: 40

“Please check whether you have got the right question paper.”

- i) Q. No. 1 is compulsory.
- ii) Attempt any two questions from remaining questions.
- iii) Assume suitable data wherever necessary.

SECTION-A

- | | | |
|-----|--|----------|
| Q.1 | Solve <u>any five</u> questions | 10 |
| | <ol style="list-style-type: none"> 1) Define inductance. Enlist the types of inductor. 2) Draw the symbols of following devices (1) TRIAC (2) n-channel DMOSFET (3) NPN Transitory (4) P-channel JFET 3) Draw the construction of MIETE opto coupler. 4) Explain the necessity of rectifier. 5) Define line regulation. Write its equation also. 6) Convert the following $(11011)_2 = ()_{10}$ 7) Draw the truth table of NAND as well as OR gate. 8) Enlist the features of IC 7400. | |
| Q.2 | <ol style="list-style-type: none"> a) Draw and explain the V-1 characteristic of p-N junction diode. b) Compare BJT and JFET. | 07 08 |
| Q.3 | <ol style="list-style-type: none"> a) Draw and explain the block diagram of regulated power supply. b) With neat circuit diagram explain the operation of half wave rectifier. Also draw input and output waveforms. | 07 08 |
| Q.4 | <ol style="list-style-type: none"> a) Explain basic logic gates in detail. b) State any four Boolean algebra, prove them using truth table. | 07 08 |
| Q.5 | Write a short note on (<u>any three</u>) | 15 |
| | <ol style="list-style-type: none"> 1) LED 2) IGBT 3) IC voltage regulations 4) Universal logic gates | |