

Total No. of Printed Pages:2

**SUBJECT CODE NO: H-346**  
**FACULTY OF SCIENCE AND TECHNOLOGY**  
**F.E. (All)**  
**Elements of Electrical Engineering**  
**(OLD)**

[Time: Two Hours]

[Max.Marks:40]

Please check whether you have got the right question paper.

N.B

- 1) Q. No. 1 is compulsory.
- 2) Solve any three questions from Q. No.2 to Q. No. 5.

Q.1 Solve any five

10

- 1) Define RTC, positive temperature coefficient.
- 2) State statement of Thevenin's theorem.
- 3) State the factor affecting the value of resistance. State the effect of temp. on resistance on
  - a) Gold
  - b) Rubber
- 4) Define mmf, magnetic flux, Reluctance
- 5) Define time constant of capacitor.
- 6) Draw the curve for capacitor voltage during the charging and discharging.
- 7) State maximum power transfer Theorem.
- 8) Define reluctance, permeability.

Q.2 Solve any two


10

- a) With the help of neat fig. explain magnetic Leakage and fringing.
- b) State and explain superposition Theorem.
- c) Derive the charging equation of the capacitor.

Q.3 Solve any two

10

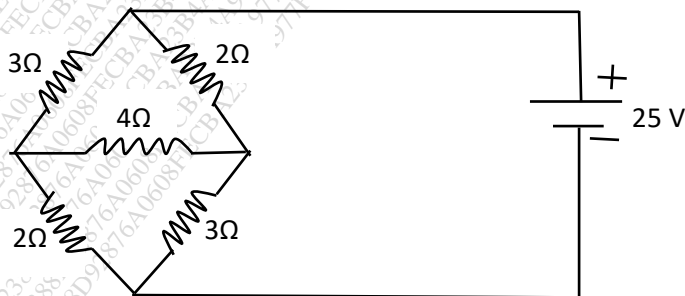- a) Find the current through  $4\Omega$  resistor by using loop Analysis.




1

H-346

b) If  $\alpha_0, \alpha_1, \alpha_2$  are temperature coefficient at  $0^\circ\text{C}, t^\circ\text{C}, t_2^\circ\text{C}$  respectively

Prove 
$$\alpha_2 = \frac{\alpha_1}{1 + \alpha_1(t_2 - t_1)}$$

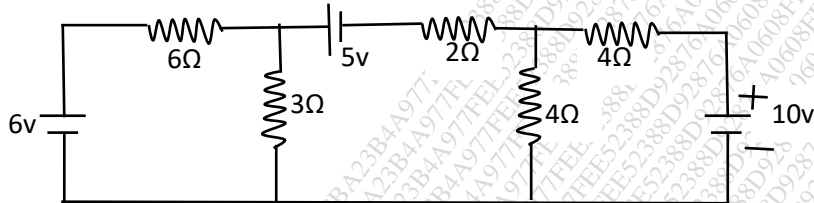c) Find current through  $3\Omega$  resistance using loop analysis.



Q.4 Solve any two.


10

- a) Explain the copper loss.
- b) Compare electric and Magnetic circuit.
- c) With neat diagram explain the concept of self and mutually induced emf.

Q.5 Solve any two.

10

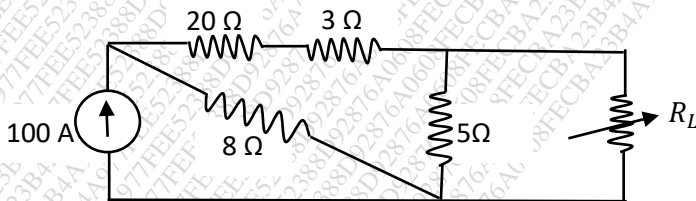- a) Compare self-inductance and mutual inductance.
- b) Find value of  $R_L$  such that maximum power transferred to it. Also find maximum power dissipated.



c) State and explain effect of temp on R.T.D.